

Coquet: A Coq library for verifying hardware

Thomas Braibant

Inria Rhône-Alpes - Université Joseph Fourier - LIG

SYNCHRON 2011

Representing circuits with predicates (or functions).

- Some definitions:

$$\mathit{Xor}(i_1, i_2, o) \triangleq (o = \neg(i_1 = i_2))$$

$$\mathit{Not}(i, o) \triangleq (o = \neg i)$$

- Adding structure:
- Correctness proof: entailment of a specification.

$$(\exists x, \mathit{Xor}(i_1, i_2, x) \wedge \mathit{Not}(x, o)) \implies (o = (i_1 = i_2))$$

Representing circuits with predicates (or functions).


- Some definitions:

$$\text{Xor}(i_1, i_2, o) \triangleq (o = \neg(i_1 = i_2))$$

$$\text{Not}(i, o) \triangleq (o = \neg i)$$

- Adding structure:

$$D(a, x) \wedge D(x, b)$$

 

- Correctness proof: entailment of a specification.

$$(\exists x, \text{Xor}(i_1, i_2, x) \wedge \text{Not}(x, o)) \implies (o = (i_1 = i_2))$$

Formalising circuits in proof assistants

Representing circuits with predicates (or functions).


- Some definitions:

$$\text{Xor}(i_1, i_2, o) \triangleq (o = \neg(i_1 = i_2))$$

$$\text{Not}(i, o) \triangleq (o = \neg i)$$

- Adding structure:

$$\exists x, D(a, x) \wedge D(x, b)$$

 

- Correctness proof: entailment of a specification.

$$(\exists x, \text{Xor}(i_1, i_2, x) \wedge \text{Not}(x, o)) \implies (o = (i_1 = i_2))$$

Representing circuits with predicates (or functions).

- Some definitions:

$$\text{Xor}(i_1, i_2, o) \triangleq (o = \neg(i_1 = i_2))$$

$$\text{Not}(i, o) \triangleq (o = \neg i)$$

- Adding structure:

Composition

$$D(a, x) \wedge D(x, b)$$

Hiding

$$\exists x, D(a, x) \wedge D(x, b)$$

- Correctness proof: entailment of a specification.

$$(\exists x, \text{Xor}(i_1, i_2, x) \wedge \text{Not}(x, o)) \implies (o = (i_1 = i_2))$$

Representing circuits with predicates (or functions).

- Some definitions:

$$\text{Xor}(i_1, i_2, o) \triangleq (o = \neg(i_1 = i_2))$$

$$\text{Not}(i, o) \triangleq (o = \neg i)$$

- Adding structure:

Composition

$$D(a, x) \wedge D(x, b)$$

Hiding

$$\exists x, D(a, x) \wedge D(x, b)$$

- Correctness proof: entailment of a specification.

$$(\exists x, \text{Xor}(i_1, i_2, x) \wedge \text{Not}(x, o)) \implies (o = (i_1 = i_2))$$

The good points of a shallow embedding


Representing circuits with predicates of the host language makes modelling of circuits easy.

- Use the binders of the theorem prover: \forall, \exists .
- Use recursion to define recursive structure:

```
let rec mux n (sel,a,b,out) = match n with
| 0   →  $\top$ 
| S n → hd out = (if sel then hd a else hd b)
      ∧ mux n (sel,tl a, tl b, tl out)
```

Use **lists** to model **bit-vectors**. We have `a, b, out: bool list`.

The bad points of a shallow embedding

 

- Let's define a recursive adder.

```
let rec adder n (a,b,cin,sum,cout) = match n with
| 0   →  $\top$ 
| S n →  $\exists c. \text{adder } n (\text{tl } a, \text{tl } b, c, \text{tl } \text{sum}, \text{cout})$ 
       $\wedge \text{add1 } (\text{hd } a, \text{hd } b, \text{cin}, \text{hd } \text{sum}, c)$ 
```

- Alternatively,

```
let adder (a,b,cin,sum,cout) =
let cout',sum' = List.fold_right2 ( $\lambda a b (c,\text{res}) \rightarrow \dots$ ) a b (cin,[]) in
sum = sum'  $\wedge$  cout = cout'
```

Question

What is a circuit ?

Shallow-Embeddings vs Deep-Embedding

Using a shallow-embedding, there is no way to:

- restrict the quantification on **circuits**;
- reason on the structure of the circuit in the proof assistant.

Move to a deep-embedding:

- define a **data structure for circuits**;
- define what's a circuit semantics (via an interpretation function);
- prove that a device implements a given specification.

Shallow-Embeddings vs Deep-Embedding

Using a shallow-embedding, there is no way to:


- restrict the quantification on **circuits**;
- reason on the structure of the circuit in the proof assistant.

Move to a deep-embedding:

- define a **data structure for circuits**;
- define what's a circuit semantics (via an interpretation function);
- prove that a device implements a given specification.

- Use Coq to embed a language for (synchronous) circuits
- Prove the functional correction of circuits


No currents, no delays

 

Fork 2 \triangleright Atom NOR

Ser 1 2 1 (Fork 2) (Atom NOR)

Gate Not : `circuit 1 1`

 

(And & One 1) \triangleright And

Ser 3 2 1 (Par 2 1 1 1 AND (One 1)) AND

Gate And3 : `circuit 3 1`

- 1 Defining a deep-embedding of circuits
- 2 Recursive circuits
- 3 Sequential circuits: time and loops
- 4 Conclusion, perspectives and related works

A dependent type for circuits in Coq

- First version:

`Inductive C : nat → nat → Type := ...`

- Examples:

`Not : C 1 1`

`And3 : C 3 1`

`Adder n : C (2n + 1) (n + 1)`

- Does not give much structure!

$$2n + 1 = n + n + 1$$

$$= n + 1 + n$$

$$= 1 + n + n$$

A dependent type for circuits in Coq

- First version:

`Inductive C : nat → nat → Type := ...`

- Examples:

`Not : C 1 1`

`And3 : C 3 1`

`Adder n : C (2n + 1) (n + 1)`

- Does not give much structure!

$$2n + 1 = n + n + 1$$

$$= n + 1 + n$$

$$= 1 + n + n$$

A better dependent type for circuits in Coq

- We use arbitrary types as **indexes** for the ports:

Inductive $\mathbb{C} : \text{Type} \rightarrow \text{Type} \rightarrow \text{Type} := \dots$

- For instance (**1** is the unit type, and \oplus is disjoint-sum):

Not : $\mathbb{C} \mathbf{1} \mathbf{1}$

And3 : $\mathbb{C} (\mathbf{1} \oplus \mathbf{1} \oplus \mathbf{1}) \mathbf{1}$

Adder n : $\mathbb{C} (n \cdot \mathbf{1} \oplus n \cdot \mathbf{1} \oplus \mathbf{1}) (n \cdot \mathbf{1} \oplus \mathbf{1})$

semantics $(\mathbf{1} \rightarrow \mathbb{B}) \rightarrow (\mathbf{1} \rightarrow \mathbb{B})$

semantics $(\mathbf{1} \oplus \mathbf{1} \oplus \mathbf{1} \rightarrow \mathbb{B}) \rightarrow (\mathbf{1} \rightarrow \mathbb{B})$

...

A better dependent type for circuits in Coq

- We use arbitrary types as **indexes** for the ports:

Inductive $\mathbb{C} : \text{Type} \rightarrow \text{Type} \rightarrow \text{Type} := \dots$

- For instance ($\mathbf{1}$ is the unit type, and \oplus is disjoint-sum):

Not : $\mathbb{C} \mathbf{1}_{i_1} \mathbf{1}_{o_1}$...

And3 : $\mathbb{C} (\mathbf{1}_{i_1} \oplus \mathbf{1}_{i_2} \oplus \mathbf{1}_{i_3}) \mathbf{1}_{o_1}$...

Adder n : $\mathbb{C} (n \cdot \mathbf{1}_a \oplus n \cdot \mathbf{1}_b \oplus \mathbf{1}_{cin}) (n \cdot \mathbf{1}_{sum} \oplus \mathbf{1}_{cout})$...

- Note. The indices are **tags**, used to identify $\mathbf{1}$. (Can use any infinite type.)

A better dependent type for circuits in Coq

- We use arbitrary types as **indexes** for the ports:

Inductive $\mathbb{C} : \text{Type} \rightarrow \text{Type} \rightarrow \text{Type} := \dots$


- For instance (**1** is the unit type, and \oplus is disjoint-sum):

Not : $\mathbb{C} \mathbf{1}_{i_1} \mathbf{1}_{o_1}$...

And3 : $\mathbb{C} (\mathbf{1}_{i_1} \oplus \mathbf{1}_{i_2} \oplus \mathbf{1}_{i_3}) \mathbf{1}_{o_1}$...

Adder n : $\mathbb{C} (n \cdot \mathbf{1}_a \oplus n \cdot \mathbf{1}_b \oplus \mathbf{1}_{cin}) (n \cdot \mathbf{1}_{sum} \oplus \mathbf{1}_{cout})$...

- Note. The indices are **tags**, used to identify **1**. (Can use any infinite type.)
- Can use other types. Compare $n : \mathbb{C} (n \cdot \mathbf{1}_a \oplus n \cdot \mathbf{1}_b)$ (CMP) where
Inductive **CMP** : **Type** := | Eq | Lt | Gt.

 

Plugs

We use **circuit combinators** ($\&$, \triangleright).

- The information flow is implicit.
- Nameless setting: ports have to be duplicated and reordered using **plugs**.
- A plug is a circuit of type $\mathbb{C} \ n \ m \ \dots$ defined as a **map** from m to n .
- Forbids short-circuits.

Example






$\mathbb{C} \ (n \oplus m) \ m$

$$\begin{array}{l} m \rightarrow n \oplus m \\ x \mapsto \text{inr } x \end{array}$$

Plugs

We use **circuit combinators** ($\&$, \triangleright).

   - The information flow is implicit.
- Nameless setting: wires have to be forked, and reordered using **plugs**.
- A plug is a circuit of type $\mathbb{C} \ n \ m \ \dots$ defined as a **map** from m to n .
- Forbids short-circuits.
- Examples:



types must be read bottom-up

a) `fun (x : m) => inr n x`

b) `fun (x : n ⊕ n) => match x with inl e => e | inr e => e end.`




c) `fun (x : p ⊕ (n ⊕ n)) => match x with
| inl ep => inr (n ⊕ m) ep
| inr (inl en) => inl p (inl m en)
| inr (inr en) => inl p (inl m en)`

by proof-search

Plugs

We use **circuit combinators** ($\&$, \triangleright).

   - The information flow is implicit.
- Nameless setting: wires have to be forked, and reordered using **plugs**.
- A plug is a circuit of type $\mathbb{C} \ n \ m \ \dots$ defined as a **map** from m to n .
- Forbids short-circuits.
- Examples:



types must be read bottom-up

- a) `fun (x : m) => inr n x`
- b) `fun (x : n ⊕ n) => match x with inl e => e | inr e => e end.`
- c) `fun (x : p ⊕ (n ⊕ n)) => match x with`
`| inl ep => inr (n ⊕ m) ep`
`| inr (inl en) => inl p (inl m en)`
`| inr (inr en) => inl p (inl m en)`

by **proof-search**

- Strongly typed syntax

Inductive $\mathbb{C} : \text{Type} \rightarrow \text{Type} \rightarrow \text{Type} :=$


| Atom : $\forall (n\ m : \text{Type}), \text{atom } n\ m \rightarrow \mathbb{C}\ n\ m$

| Plug : $\forall (n\ m : \text{Type}) (f : m \rightarrow n), \mathbb{C}\ n\ m$

| Ser : $\forall (n\ m\ p : \text{Type}), \mathbb{C}\ n\ m \rightarrow \mathbb{C}\ m\ p \rightarrow \mathbb{C}\ n\ p$

| Par : $\forall (n\ m\ p\ q : \text{Type}), \mathbb{C}\ n\ p \rightarrow \mathbb{C}\ m\ q \rightarrow \mathbb{C}\ (n \oplus m)\ (p \oplus q)$

| Loop : $\forall (n\ m\ p : \text{Type}), \mathbb{C}\ (n \oplus p)\ (m \oplus p) \rightarrow \mathbb{C}\ n\ m.$

 

- Intrinsic approach: an alternative to syntax + typing judgement.

The semantics of a circuit

For a circuit of type $\mathbb{C} \ n \ m$, a relation between $n \rightarrow \mathbb{T}$ and $m \rightarrow \mathbb{T}$.

Rules

$$\text{KSER} \frac{x \vdash_m^n \text{ins} \bowtie \text{middle} \quad y \vdash_p^m \text{middle} \bowtie \text{outs}}{x \triangleright y \vdash_p^n \text{ins} \bowtie \text{outs}}$$

$$\text{KPAR} \frac{x \vdash_p^n \text{left ins} \bowtie \text{left outs} \quad y \vdash_q^m \text{right ins} \bowtie \text{right outs}}{x \& y \vdash_{p \oplus q}^{n \oplus m} \text{ins} \bowtie \text{outs}}$$

$$\text{KPLUG} \frac{}{\text{Plug } f \vdash_m^n \text{ins} \bowtie \text{lift } f \text{ ins}}$$

$$\text{KLOOP} \frac{x \vdash_{m \oplus p}^{n \oplus p} \text{app ins } r \bowtie \text{app outs } r}{\text{Loop } x \vdash_m^n \text{ins} \bowtie \text{outs}}$$

Parametric in the base doors, the type \mathbb{T} and the semantics of the base doors.

Operations

Definition $\text{left } n \ m : ((n \oplus m) \rightarrow \mathbb{T}) \rightarrow (n \rightarrow \mathbb{T}) := \dots$

Definition $\text{app } n \ m : (n \rightarrow \mathbb{T}) \rightarrow (m \rightarrow \mathbb{T}) \rightarrow (n \oplus m \rightarrow \mathbb{T}) := \dots$

Definition $\text{lift } n \ m \ m (f : m \rightarrow n) (\text{ins} : n \rightarrow \mathbb{T}) : (m \rightarrow \mathbb{T}) := \text{ins} \circ f.$

The need for abstraction

The semantics of a circuit defines precisely its behavior, but:

- is **too precise** (may leak some internal details);
- is a relation between two functions $n \rightarrow \mathbb{T}$ and $m \rightarrow \mathbb{T}$. (Example: $\mathbf{1} \oplus \mathbf{1} \rightarrow \mathbb{B} \dots$).

Use **type isomorphisms** as “lenses”:

```
Class Iso (A B : Type) := {  
  iso : A → B;  
  uniso : B → A}.
```

```
Class Iso_Props {A B : Type} (I : Iso A B) := {  
  iso_uniso : ∀ (x : B), iso (uniso x) = x;  
  uniso_iso : ∀ (x : A), uniso (iso x) = x}.
```

Examples:

$$\begin{array}{c} \iota_x \\ \hline \mathbf{1}_x \rightarrow \mathbb{T} \cong \mathbb{T} \end{array} \quad \bullet \bullet \quad \frac{A \rightarrow \mathbb{T} \cong \sigma \quad B \rightarrow \mathbb{T} \cong \tau}{A \oplus B \rightarrow \mathbb{T} \cong (\sigma \times \tau)} \quad \frac{A \rightarrow \mathbb{T} \cong \sigma}{n \cdot A \rightarrow \mathbb{T} \cong \text{vector } \sigma \ n}$$

The need for abstraction

The semantics of a circuit defines precisely its behavior, but:

- is **too precise** (may leak some internal details);
- is a relation between two functions $n \rightarrow \mathbb{T}$ and $m \rightarrow \mathbb{T}$. (Example: $\mathbf{1} \oplus \mathbf{1} \rightarrow \mathbb{B} \dots$).

Use **type isomorphisms** as “lenses”:

```
Class Iso (A B : Type) := {  
  iso : A → B;  
  uniso : B → A}.
```

```
Class Iso_Props {A B : Type} (I : Iso A B) := {  
  iso_uniso : ∀ (x : B), iso (uniso x) = x;  
  uniso_iso : ∀ (x : A), uniso (iso x) = x}.
```

Examples:

$$\begin{array}{c} \iota_x \frac{}{\mathbf{1}_x \rightarrow \mathbb{T} \cong \mathbb{T}} \quad \bullet \bullet \bullet \frac{A \rightarrow \mathbb{T} \cong \sigma \quad B \rightarrow \mathbb{T} \cong \tau}{A \oplus B \rightarrow \mathbb{T} \cong (\sigma \times \tau)} \quad \frac{A \rightarrow \mathbb{T} \cong \sigma}{n \cdot A \rightarrow \mathbb{T} \cong \text{vector } \sigma \ n} \end{array}$$

Putting it all together

We define **type classes** for abstractions (and modular proofs).

Useful for proof automation

Context $(n\ m\ N\ M : \text{Type}) (Rn : (n \rightarrow \mathbb{T}) \cong N) (Rm : (m \rightarrow \mathbb{T}) \cong M)$.

Class **Realise** $(c : \mathbb{C}\ n\ m) (R : N \rightarrow M \rightarrow \text{Prop}) :=$
 $\text{realise} : \forall \text{ ins outs}, c \vdash_m^n \text{ ins} \bowtie \text{ outs} \rightarrow R (Rn.\text{iso ins}) (Rm.\text{iso outs})$.


Class **Implement** $(c : \mathbb{C}\ n\ m) (f : N \rightarrow M) :=$
 $\text{implement} : \forall \text{ ins outs}, c \vdash_m^n \text{ ins} \bowtie \text{ outs} \rightarrow Rm.\text{iso outs} = f (Rn.\text{iso ins})$.

“Up-to isomorphisms, a given circuit implements a given function.”

A complete example

Definition $\text{HADD} : \mathbb{C} (1_a \oplus 1_b) (1_s \oplus 1_c) :=$
 $\text{Fork } 2 (1_a \oplus 1_b) \triangleright (\text{XOR } a \ b \ s \ \& \ \text{AND } a \ b \ c).$

 Definition $\text{hadd} := \lambda (a,b).(a \otimes b, a \wedge b)$



Lemma $\text{HADD_Spec} : \text{Implement}$

$(t_a \bullet t_b)$
 $(t_s \bullet t_c)$
 $\text{HADD hadd}.$

$I : 1_a \oplus 1_b \rightarrow \mathbb{B}, O : 1_s \oplus 1_c \rightarrow \mathbb{B}$
 $M : (1_a \oplus 1_b) \oplus (1_a \oplus 1_b) \rightarrow \mathbb{B}$
 $\text{H0} : \text{iso } M = (\text{fun } x \Rightarrow (x,x)) (\text{iso } I)$
 $\text{H1} : \text{iso } (\text{left } O) = \text{uncurry } \otimes (\text{iso } (\text{left } M))$
 $\text{H2} : \text{iso } (\text{right } O) = \text{uncurry } \wedge (\text{iso } (\text{right } M))$
 =====
 $\text{iso } O = \text{hadd } (\text{iso } I)$

$I : 1_a \oplus 1_b \rightarrow \mathbb{B}, O : 1_s \oplus 1_c \rightarrow \mathbb{B}$

$\text{H} : \text{HADD} \vdash_{1_s \oplus 1_c}^{1_a \oplus 1_b} I \triangleright O$


=====
 $@\text{iso } (t_s \bullet t_c) O = \text{hadd } (@\text{iso } (t_a \bullet t_b) I)$

$I : \mathbb{B} * \mathbb{B}, O : \mathbb{B} * \mathbb{B},$
 $M : (\mathbb{B} * \mathbb{B}) * (\mathbb{B} * \mathbb{B}),$
 $\text{H0} : M = (\text{fun } x \Rightarrow (x,x)) I$
 $\text{H1} : \text{fst } O = \text{uncurry } \otimes (\text{fst } M)$
 $\text{H2} : \text{snd } O = \text{uncurry } \wedge (\text{snd } M)$
 =====
 $O = \text{hadd } I$

A complete example

Definition $\text{HADD} : \mathbb{C} (1_a \oplus 1_b) (1_s \oplus 1_c) :=$
 $\text{Fork } 2 (1_a \oplus 1_b) \triangleright (\text{XOR } a \ b \ s \ \& \ \text{AND } a \ b \ c).$

 Definition $\text{hadd} := \lambda (a,b).(a \otimes b, a \wedge b)$



Lemma $\text{HADD_Spec} : \text{Implement}$

$(\iota_a \bullet \iota_b)$

$(\iota_s \bullet \iota_c)$

$\text{HADD } \text{hadd}.$

$I : 1_a \oplus 1_b \rightarrow \mathbb{B}, O : 1_s \oplus 1_c \rightarrow \mathbb{B}$

$M : (1_a \oplus 1_b) \oplus (1_a \oplus 1_b) \rightarrow \mathbb{B}$

$H0: \text{iso } M = (\text{fun } x \Rightarrow (x,x)) (\text{iso } I)$

$H1: \text{iso } (\text{left } O) = \text{uncurry } \otimes (\text{iso } (\text{left } M))$

$H2: \text{iso } (\text{right } O) = \text{uncurry } \wedge (\text{iso } (\text{right } M))$

=====

$\text{iso } O = \text{hadd } (\text{iso } I)$

$I : 1_a \oplus 1_b \rightarrow \mathbb{B}, O : 1_s \oplus 1_c \rightarrow \mathbb{B}$

$H : \text{HADD} \vdash_{1_a \oplus 1_b}^{1_s \oplus 1_c} I \triangleright O$

=====

$@\text{iso } (\iota_s \bullet \iota_c) O = \text{hadd } (@\text{iso } (\iota_a \bullet \iota_b) I)$

$I : \mathbb{B} * \mathbb{B}, O : \mathbb{B} * \mathbb{B},$

$M : (\mathbb{B} * \mathbb{B}) * (\mathbb{B} * \mathbb{B}),$

$H0: M = (\text{fun } x \Rightarrow (x,x)) I$

$H1: \text{fst } O = \text{uncurry } \otimes (\text{fst } M)$

$H2: \text{snd } O = \text{uncurry } \wedge (\text{snd } M)$

=====

$O = \text{hadd } I$

A complete example

Definition $\text{HADD} : \mathbb{C} (\mathbf{1}_a \oplus \mathbf{1}_b) (\mathbf{1}_s \oplus \mathbf{1}_c) :=$
 $\text{Fork } 2 (\mathbf{1}_a \oplus \mathbf{1}_b) \triangleright (\text{XOR } a \ b \ s \ \& \ \text{AND } a \ b \ c).$

Definition $\text{hadd} := \lambda (a,b).(a \otimes b, a \wedge b)$

Lemma $\text{HADD_Spec} : \text{Implement}$

$(\iota_a \bullet \iota_b)$

$(\iota_s \bullet \iota_c)$

$\text{HADD } \text{hadd}.$

$I : \mathbf{1}_a \oplus \mathbf{1}_b \rightarrow \mathbb{B}, O : \mathbf{1}_s \oplus \mathbf{1}_c \rightarrow \mathbb{B}$

$M : (\mathbf{1}_a \oplus \mathbf{1}_b) \oplus (\mathbf{1}_a \oplus \mathbf{1}_b) \rightarrow \mathbb{B}$


$H0 : \text{iso } M = (\text{fun } x \Rightarrow (x,x)) (\text{iso } I)$

$H1 : \text{iso } (\text{left } O) = \text{uncurry } \otimes (\text{iso } (\text{left } M))$

$H2 : \text{iso } (\text{right } O) = \text{uncurry } \wedge (\text{iso } (\text{right } M))$

=====

 $\text{iso } O = \text{hadd } (\text{iso } I)$



$I : \mathbf{1}_a \oplus \mathbf{1}_b \rightarrow \mathbb{B}, O : \mathbf{1}_s \oplus \mathbf{1}_c \rightarrow \mathbb{B}$

$H : \text{HADD} \vdash_{\mathbf{1}_s \oplus \mathbf{1}_c}^{\mathbf{1}_a \oplus \mathbf{1}_b} I \triangleleft O$

=====

$@\text{iso } (\iota_s \bullet \iota_c) O = \text{hadd } (@\text{iso } (\iota_a \bullet \iota_b) I)$

$I : \mathbb{B} * \mathbb{B}, O : \mathbb{B} * \mathbb{B},$

$M : (\mathbb{B} * \mathbb{B}) * (\mathbb{B} * \mathbb{B}),$

$H0 : M = (\text{fun } x \Rightarrow (x,x)) I$

$H1 : \text{fst } O = \text{uncurry } \otimes (\text{fst } M)$

$H2 : \text{snd } O = \text{uncurry } \wedge (\text{snd } M)$


=====

$O = \text{hadd } I$

A complete example

Definition $\text{HADD} : \mathbb{C} (\mathbf{1}_a \oplus \mathbf{1}_b) (\mathbf{1}_s \oplus \mathbf{1}_c) :=$
 $\text{Fork } 2 (\mathbf{1}_a \oplus \mathbf{1}_b) \triangleright (\text{XOR } a \ b \ s \ \& \ \text{AND } a \ b \ c).$

 Definition $\text{hadd} := \lambda (a,b).(a \otimes b, a \wedge b)$



Lemma $\text{HADD_Spec} : \text{Implement}$

$(\iota_a \bullet \iota_b)$

$(\iota_s \bullet \iota_c)$

$\text{HADD } \text{hadd}.$

$I : \mathbf{1}_a \oplus \mathbf{1}_b \rightarrow \mathbb{B}, O : \mathbf{1}_s \oplus \mathbf{1}_c \rightarrow \mathbb{B}$

$M : (\mathbf{1}_a \oplus \mathbf{1}_b) \oplus (\mathbf{1}_a \oplus \mathbf{1}_b) \rightarrow \mathbb{B}$

$H0 : \text{iso } M = (\text{fun } x \Rightarrow (x,x)) (\text{iso } I)$

$H1 : \text{iso } (\text{left } O) = \text{uncurry } \otimes (\text{iso } (\text{left } M))$

$H2 : \text{iso } (\text{right } O) = \text{uncurry } \wedge (\text{iso } (\text{right } M))$

=====

$\text{iso } O = \text{hadd } (\text{iso } I)$

$I : \mathbf{1}_a \oplus \mathbf{1}_b \rightarrow \mathbb{B}, O : \mathbf{1}_s \oplus \mathbf{1}_c \rightarrow \mathbb{B}$

$H : \text{HADD} \vdash_{\mathbf{1}_s \oplus \mathbf{1}_c}^{\mathbf{1}_a \oplus \mathbf{1}_b} I \triangleleft O$

=====

$@\text{iso } (\iota_s \bullet \iota_c) O = \text{hadd } (@\text{iso } (\iota_a \bullet \iota_b) I)$

$I : \mathbb{B} * \mathbb{B}, O : \mathbb{B} * \mathbb{B},$

$M : (\mathbb{B} * \mathbb{B}) * (\mathbb{B} * \mathbb{B}),$

$H0 : M = (\text{fun } x \Rightarrow (x,x)) I$

$H1 : \text{fst } O = \text{uncurry } \otimes (\text{fst } M)$

$H2 : \text{snd } O = \text{uncurry } \wedge (\text{snd } M)$


=====

$O = \text{hadd } I$

A complete example

Definition $\text{HADD} : \mathbb{C} (\mathbf{1}_a \oplus \mathbf{1}_b) (\mathbf{1}_s \oplus \mathbf{1}_c) :=$
 $\text{Fork } 2 (\mathbf{1}_a \oplus \mathbf{1}_b) \triangleright (\text{XOR } a \ b \ s \ \& \ \text{AND } a \ b \ c).$

 Definition $\text{hadd} := \lambda (a,b).(a \otimes b, a \wedge b)$



Lemma $\text{HADD_Spec} : \text{Implement}$

$(\iota_a \bullet \iota_b)$

$(\iota_s \bullet \iota_c)$

$\text{HADD } \text{hadd}.$

$I : \mathbf{1}_a \oplus \mathbf{1}_b \rightarrow \mathbb{B}, O : \mathbf{1}_s \oplus \mathbf{1}_c \rightarrow \mathbb{B}$

$M : (\mathbf{1}_a \oplus \mathbf{1}_b) \oplus (\mathbf{1}_a \oplus \mathbf{1}_b) \rightarrow \mathbb{B}$

$H0 : \text{iso } M = (\text{fun } x \Rightarrow (x,x)) (\text{iso } I)$

$H1 : \text{iso } (\text{left } O) = \text{uncurry } \otimes (\text{iso } (\text{left } M))$

$H2 : \text{iso } (\text{right } O) = \text{uncurry } \wedge (\text{iso } (\text{right } M))$

=====

$\text{iso } O = \text{hadd } (\text{iso } I)$

$I : \mathbf{1}_a \oplus \mathbf{1}_b \rightarrow \mathbb{B}, O : \mathbf{1}_s \oplus \mathbf{1}_c \rightarrow \mathbb{B}$

$H : \text{HADD } \vdash_{\mathbf{1}_a \oplus \mathbf{1}_b}^{\mathbf{1}_s \oplus \mathbf{1}_c} I \triangleright O$

=====

$@\text{iso } (\iota_s \bullet \iota_c) O = \text{hadd } (@\text{iso } (\iota_a \bullet \iota_b) I)$

$I : \mathbb{B} * \mathbb{B}, O : \mathbb{B} * \mathbb{B},$

$M : (\mathbb{B} * \mathbb{B}) * (\mathbb{B} * \mathbb{B}),$

$H0 : M = (\text{fun } x \Rightarrow (x,x)) I$

$H1 : \text{fst } O = \text{uncurry } \otimes (\text{fst } M)$

$H2 : \text{snd } O = \text{uncurry } \wedge (\text{snd } M)$


=====

$O = \text{hadd } I$

A complete example

Definition $\text{HADD} : \mathbb{C} (1_a \oplus 1_b) (1_s \oplus 1_c) :=$
 $\text{Fork } 2 (1_a \oplus 1_b) \triangleright (\text{XOR } a \ b \ s \ \& \ \text{AND } a \ b \ c).$

 Definition $\text{hadd} := \lambda (a,b).(a \otimes b, a \wedge b)$



Lemma $\text{HADD_Spec} : \text{Implement}$

$(\iota_a \bullet \iota_b)$
 $(\iota_s \bullet \iota_c)$
 $\text{HADD hadd}.$

$I : 1_a \oplus 1_b \rightarrow \mathbb{B}, O : 1_s \oplus 1_c \rightarrow \mathbb{B}$
 $M : (1_a \oplus 1_b) \oplus (1_a \oplus 1_b) \rightarrow \mathbb{B}$
 $\text{H0} : \text{iso } M = (\text{fun } x \Rightarrow (x,x)) (\text{iso } I)$
 $\text{H1} : \text{iso } (\text{left } O) = \text{uncurry } \otimes (\text{iso } (\text{left } M))$
 $\text{H2} : \text{iso } (\text{right } O) = \text{uncurry } \wedge (\text{iso } (\text{right } M))$
 $\text{iso } O = \text{hadd } (\text{iso } I)$

$I : 1_a \oplus 1_b \rightarrow \mathbb{B}, O : 1_s \oplus 1_c \rightarrow \mathbb{B}$

$\text{H} : \text{HADD} \vdash_{1_s \oplus 1_c}^{1_a \oplus 1_b} I \triangleright O$

$\text{@iso } (\iota_s \bullet \iota_c) O = \text{hadd } (\text{@iso } (\iota_a \bullet \iota_b) I)$

$I : \mathbb{B} * \mathbb{B}, O : \mathbb{B} * \mathbb{B},$
 $M : (\mathbb{B} * \mathbb{B}) * (\mathbb{B} * \mathbb{B}),$
 $\text{H0} : M = (\text{fun } x \Rightarrow (x,x)) I$
 $\text{H1} : \text{fst } O = \text{uncurry } \otimes (\text{fst } M)$
 $\text{H2} : \text{snd } O = \text{uncurry } \wedge (\text{snd } M)$
 $O = \text{hadd } I$

- 1 Defining a deep-embedding of circuits
- 2 Recursive circuits**
- 3 Sequential circuits: time and loops
- 4 Conclusion, perspectives and related works

n -bit integers

Record $\mathbb{W}_n := \text{mk_word } \{\text{val} : \mathbb{Z}; \text{range}: 0 \leq \text{val} < 2^n\}$.

Definition $\text{repr } n : \mathbb{Z} \rightarrow \mathbb{W}_n := \dots$

Definition $\text{high } n \ m : \mathbb{W}_{(n+m)} \rightarrow \mathbb{W}_m := \dots$

Definition $\text{low } n \ m : \mathbb{W}_{(n+m)} \rightarrow \mathbb{W}_n := \dots$


Definition $\text{combine } n \ m : \mathbb{W}_n \rightarrow \mathbb{W}_m \rightarrow \mathbb{W}_{(n+m)} := \dots$

Definition $\text{carry_add } n \ (x \ y : \mathbb{W}_n) \ (b : \mathbb{B}) : \mathbb{W}_n * \mathbb{B} :=$

$\text{let } e := \text{val } x + \text{val } y + (\text{if } b \text{ then } 1 \text{ else } 0) \text{ in } (e \bmod 2^n, 2^n \leq e)$

Definition $\Phi_x^n : (n \cdot \mathbf{1}_x \rightarrow \mathbb{B}) \cong (\mathbb{W}_n) := \dots$

A 1-bit adder

 

Instance FADD_1 : Implement

$(\iota_{cin} \bullet (\iota_a \bullet \iota_b))$

$(\iota_{sum} \bullet \iota_{cout})$

FADD

$(\text{fun } (c, (x, y)) \Rightarrow (x \oplus (y \oplus c), (x \wedge y) \vee c \wedge (x \oplus y)))$.

Context a b cin sum cout : string.

Program Definition FADD :

```
C (1cin ⊕ (1a ⊕ 1b)) (1sum ⊕ 1cout) :=
(ONE 1cin & HADD a b "s1" "c1")
▷ ...
▷ (HADD cin "s1" sum "c2" & ONE 1c1)
▷ ...
▷ (ONE 1sum & OR "c2" "c1" cout).
```

Instance FADD_2 : Implement


$(\iota_{cin} \bullet (\Phi_a^1 \bullet \Phi_b^1))$

$(\Phi_{sum}^1 \bullet \iota_{cout})$

FADD

$(\text{fun } (c, (x, y)) \Rightarrow \text{carry_add } 1 \ x \ y \ c)$.

A n -bit adder

 

Program Fixpoint ADD cin a b cout sum n :

$\mathbb{C} (\mathbf{1}_{\text{cin}} \oplus n \cdot \mathbf{1}_a \oplus n \cdot \mathbf{1}_b) (n \cdot \mathbf{1}_{\text{sum}} \oplus \mathbf{1}_{\text{cout}}) :=$

match n with

| 0 \Rightarrow ...

| S p \Rightarrow ... \triangleright (ONE $(\mathbf{1}_{\text{cin}})$ & HIGHLOWS a b 1 p)

\triangleright ... \triangleright (FADD a b cin sum "c" & ONE $(p \cdot \mathbf{1}_a \oplus p \cdot \mathbf{1}_b)$)

\triangleright ... \triangleright (ONE $(\mathbf{1}_{\text{sum}})$ & ADD "c" a b cout s p)

\triangleright ... \triangleright COMBINE sum 1 p & ONE $(\mathbf{1}_{\text{cout}})$

end.

Lemma add_parts n m (xH yH : \mathbb{W}_m) (xL yL : \mathbb{W}_n) cin:

let (sumL,middle) := carry_add n xL yL cin in

let (sumH,cout) := carry_add m xH yH middle in

let sum := combine n m sumL sumH in

carry_add (n + m) (combine n m xL xH)(combine n m yL yH) cin = (sum,cout).

Instance ADD_Spec cin a b cout sum n : Implement


$(\iota_{\text{cin}} \bullet (\Phi_a^n \bullet \Phi_b^n))$

$(\Phi_{\text{sum}}^n \bullet \iota_{\text{cout}})$

(ADD cin a b cout sum n)

(fun (c,(x,y)) \Rightarrow carry_add c x y).

Some sub-components

 

Definition $HL\ x\ n\ p : \mathbb{C} ((n + p) \cdot \mathbf{1}_x) (n \cdot \mathbf{1}_x \oplus p \cdot \mathbf{1}_x) := \text{Plug ...}$

Definition $COMBINE\ x\ n\ p : \mathbb{C} (n \cdot \mathbf{1}_x \oplus p \cdot \mathbf{1}_x) ((n + p) \cdot \mathbf{1}_x) := \text{Plug ...}$

Instance $HL_Spec\ x\ n\ p : \text{Implement}$



$(\Phi_x^{n+p}) (\Phi_x^n \bullet \Phi_x^p) (HL\ x\ n\ p) (\text{fun } x \Rightarrow (\text{low } n\ p\ x, \text{high } n\ p\ x)).$

Instance $COMBINE_Spec\ x\ n\ p : \text{Implement}$

$(\Phi_x^n \bullet \Phi_x^p) (\Phi_x^{n+p}) (COMBINE\ x\ n\ p) (\text{fun } x \Rightarrow (\text{combine } n\ p\ (\text{fst } x)\ (\text{snd } x))).$

A divide and conquer adder

  - Add in **parallel** the high-order **and** the low-order bits.
- Computes s (resp. t) the sum without (resp. with) a carry-in
- Computes p the **carry-propagate** and g the **carry-generate**





Implements the following Coq (high-level) function:

```
Definition dc n : W2n * W2n → B * B * W2n * W2n := fun (x,y) =>
let (s,g) := carry_add 2n x y false in
let (t,p) := carry_add 2n x y true in (g,p,s,t).
```

A divide and conquer adder

 
 
- Add in **parallel** the high-order **and** the low-order bits.
- Computes s (resp. t) the sum without (resp. with) a carry-in
- Computes p the **carry-propagate** and g the **carry-generate**



Implements the following Coq (high-level) function:

```
Definition dc n : W2n * W2n → B * B * W2n * W2n := fun (x,y) =>
let (s,g) := carry_add 2n x y false in
let (t,p) := carry_add 2n x y true in (g,p,s,t).
```

A divide and conquer adder

  

Implements the following Coq (high-level) function:

```
Definition dc n : W2n * W2n → B * B * W2n * W2n := fun (x,y) =>  
let (s,g) := carry_add 2n x y false in  
let (t,p) := carry_add 2n x y true in (g,p,s,t).
```

- The high-level specification says **nothing** of the computational behavior of the circuit.
- The deep-embedding makes it possible to study the **latency** of this circuit.

- 1 Defining a deep-embedding of circuits
- 2 Recursive circuits
- 3 Sequential circuits: time and loops**
- 4 Conclusion, perspectives and related works

Streams

In this section \mathbb{T} is stream \mathbb{B} i.e., $\text{nat} \rightarrow \mathbb{B}$.

We have several interesting isomorphisms:

Definition `Iso_stream A B C (I: (A → B) ≅ C) : (A → stream B) ≅ (stream C) := ...`

Definition `Iso_prod_stream : (stream A * stream B) ≅ (stream (A * B)) := ...`

Definition `Iso_vector_stream n : (vector (stream A) n) ≅ (stream (vector A n)) := ...`

Examples:

$(\mathbf{1} \oplus \mathbf{1} \rightarrow \text{nat} \rightarrow \mathbb{B}) \cong (\text{stream } (\mathbb{B} * \mathbb{B}))$

$(n \cdot \mathbf{1} \rightarrow \text{nat} \rightarrow \mathbb{B}) \cong (\text{stream } (\mathbb{W}_n))$

We assume (through appropriate parametrization) a gate DFF that implements a pre:

Definition `pre {A} (d : A):
stream A → stream A := fun f t =>
match t with | 0 => d | S p => f p end.`

Instance `DFF_Realise_stream (a out):
Implement (DFF a out) (ta) (tout)
(pre false).`

Not in this talk: buffers defined with circuit combinators

Streams

In this section \mathbb{T} is stream \mathbb{B} i.e., $\text{nat} \rightarrow \mathbb{B}$.

We have several interesting isomorphisms:

Definition `Iso_stream A B C (I: (A → B) ≅ C) : (A → stream B) ≅ (stream C) := ...`

Definition `Iso_prod_stream : (stream A * stream B) ≅ (stream (A * B)) := ...`

Definition `Iso_vector_stream n : (vector (stream A) n) ≅ (stream (vector A n)) := ...`

Examples:

`(1 ⊕ 1 → nat → ℤ) ≅ (stream (ℤ * ℤ))`

`(n · 1 → nat → ℤ) ≅ (stream (ℚn))`

We assume (through appropriate parametrization) a gate DFF that implements a pre:

Definition `pre {A} (d : A):
stream A → stream A := fun f t ⇒
match t with | 0 ⇒ d | S p ⇒ f p end.`

Instance `DFF_Realise_stream {a out}:
Implement (DFF a out) (ℓa) (ℓout)
(pre false).`

Not in this talk: buffers defined with circuit combinators

Well-behaved circuits

“Circuits that have the same behavior in the boolean setting and pointwise in a stream”

A well-behaved atom satisfies:

$$\forall ins, \forall outs, \text{stream } \mathbb{B} \models ins \bowtie outs \implies \forall t, \mathbb{B} \models ins@t \bowtie outs@t.$$

Plugs are well-behaved, as well as parallel and serial circuits when their sub-circuits are well-behaved.

Lifting

Lemma `lifting_map n m x (Hwf: wb n m x) N M`

`(Rn : (n → B) ≅ N)`

`(Rm : (m → B) ≅ M)`

`(f : N → M):`


`Implement B ... Rn Rm x f →`

`Implement (stream B) ... (Iso_stream Rn) (Iso_stream Rm) x (Stream.map f).`

A memory element

We can also deal with state-holding structures:

 Definition REGISTER: $\mathbb{C} (\mathbf{1}_{load} \oplus \mathbf{1}_a) \mathbf{1}_{out} :=$
Loop $(\mathbf{1}_{load} \oplus \mathbf{1}_a) \mathbf{1}_{out} \mathbf{1}_{out}$
 (Plug ... \triangleright MUX2 a out load "in_dff"
 \triangleright DFF "in_dff" out
 \triangleright Fork 2 $\mathbf{1}_{out}$).



This circuit realise the following relation:

Record reg_ti := {va : bool; vload : bool}.

Instance Register_Spec : Realise (... : $\mathbf{1}_{load} \oplus \mathbf{1}_a \rightarrow \text{stream } \mathbb{B} \cong \text{stream reg_ti}$) (t_{out}) REGISTER
(fun ins outs \Rightarrow outs = pre false (fun t \Rightarrow if (ins t).(vload) then (ins t).(va) else outs t)).


Note

Relations on streams are not the nicest way to reason about state-holding devices.

A memory element

We can also deal with state-holding structures:
 
```
Definition REGISTER: C (1load ⊕ 1a) 1out :=  
Loop (1load ⊕ 1a) 1out 1out  
  (Plug ... ▷ MUX2 a out load "in_dff"  
   ▷ DFF "in_dff" out  
   ▷ Fork 2 1out).
```



This circuit realise the following relation:

```
Record reg_ti := {va : bool; vload : bool}.
```

```
Instance Register_Spec : Realise (... : 1load ⊕ 1a → stream B ≅ stream reg_ti) (tout) REGISTER  
  (fun ins outs ⇒ outs = pre false (fun t ⇒ if (ins t).(vload) then (ins t).(va) else outs t)).
```


Note

Relations on streams are not the nicest way to reason about state-holding devices.

A memory element

We can also deal with state-holding structures:
 
```
Definition REGISTER: C (1load ⊕ 1a) 1out :=  
Loop (1load ⊕ 1a) 1out 1out  
  (Plug ... ▷ MUX2 a out load "in_dff"  
   ▷ DFF "in_dff" out  
   ▷ Fork 2 1out).
```



This circuit realise the following relation:

```
Record reg_ti := {va : bool; vload : bool}.
```

```
Instance Register_Spec : Realise (... : 1load ⊕ 1a → stream B ≅ stream reg_ti) (tout) REGISTER  
  (fun ins outs ⇒ outs = pre false (fun t ⇒ if (ins t).(vload) then (ins t).(va) else outs t)).
```

Note

Relations on streams are not the nicest way to reason about state-holding devices.

Using Moore automata as specifications


Record Moore I O σ := { λ : $\sigma \rightarrow O$; δ : $\sigma \rightarrow I \rightarrow \sigma$ }.

Fixpoint iterate (M: Moore I O σ) (x: σ) (ins: stream I) (k: nat): σ :=
 match k with | 0 \Rightarrow x | S n \Rightarrow M. (δ) (iterate M x ins n) (ins n) **end**.

Definition outputs (M: Moore I O σ) (x: σ) (ins: nat \rightarrow I) k : O := M. (λ) (iterate M x ins k).

A memory element (cont)

 Definition REGISTER: $\mathbb{C} (\mathbf{1}_{\text{load}} \oplus \mathbf{1}_a) \mathbf{1}_{\text{out}} :=$
Loop $(\mathbf{1}_{\text{load}} \oplus \mathbf{1}_a) \mathbf{1}_{\text{out}} \mathbf{1}_{\text{out}}$
 (Plug ... \triangleright MUX2 a out load "in_dff"
 \triangleright DFF "in_dff" out
 \triangleright Fork 2 $\mathbf{1}_{\text{out}}$).



Record reg_ti := {va : bool; vload : bool}.

Definition reg_m : Moore reg_ti bool bool :=
{| $\lambda := \text{id}; \delta := \text{fun state ins} \Rightarrow \text{if ins.(vload) then ins.(va) else state}$ }.

Instance Register_Spec : Realise (... : $\mathbf{1}_{\text{load}} \oplus \mathbf{1}_a \rightarrow \text{stream } \mathbb{B} \cong \text{stream reg_ti}$) (ι_{out}) REGISTER
(fun ins outs \Rightarrow outs = Moore.outputs reg_m false ins).

Simulation:

- This first-order encoding makes it possible to simulate circuits inside Coq.
- It requires a computational interpretation of each basic gate.

Variable `sem : $\forall a b, \text{atom } a b \rightarrow (a \rightarrow \mathbb{T}) \rightarrow \text{option } (b \rightarrow \mathbb{T})$.`

Fixpoint `simulation n m (c : circuit atom n m) : (n \rightarrow \mathbb{T}) \rightarrow option (m \rightarrow \mathbb{T}) := ...`

- Not very efficient...

Using the same idea:

- computation of the gate-count and length of the critical path;
- **pretty-printing** of the list of gates (and their connection).

Almost to VHDL

Conclusion

- A deep-embedding of circuits in Coq
- Build and reason about circuits, proving high-level specifications through type-isomorphisms
- Dependent types are useful to capture some well-formedness properties
- Examples: arithmetic circuits of parametric size, proved by induction

- Verifying circuits with theorem provers:
 - in HOL or in Coq, mainly shallow-embeddings;
 - in HOL, a compiler from HOL to VHDL;
 - in ACL2, shallow-embeddings (up to a microprocessor), not higher-order.
 - in PVS, a shallow-embedding of a pipelined micro-processor
- Algebraic definitions of circuits:
 - Lafont: algebraic theory of boolean circuits.
 - Hinze: the algebra of parallel prefix circuits.
- Functional languages in hardware design:
 - Many approaches based on circuits combinators (often lack dependent types)
 - **Lava**: language embedded in Haskell to describe circuits (combinator based, but use names for wires)

- More arithmetic circuits.
- Transformations.
- Some front-end to generate circuits.

When I am PhDone:

```
Inductive aexp : nat → Type :=
| AVar: ∀ n (i : Var E n), aexp n
| AConst: ∀ n, Word.word n → aexp n
| APlus: ∀ n, aexp n → aexp n → aexp n
| ALO: ∀ n m, aexp (n + m) → aexp n
| AHi: ∀ n m, aexp (n + m) → aexp m
| ACat: ∀ n m, aexp n → aexp m → aexp (n + m).
```

```
Inductive bexp : Type :=
| BTrue: bexp
| BFalse: bexp
| BEq: ∀ n, aexp n → aexp n → bexp
| BLt: ∀ n, aexp n → aexp n → bexp
| BNot: bexp → bexp
| BAnd: bexp → bexp → bexp.
```

```
Inductive com (E: list nat) : Type :=
| CSkip: com E
| CAss: ∀ n (v : Var E n), aexp E n → com E
| CSeq: com E → com E → com E
| CIf: bexp E → com E → com E → com E
| CWhile: bexp E → com E → com E
| CNew: ∀ n, aexp E n → com (snoc E n) → com E
```

- More arithmetic circuits.
- Transformations.
- Some front-end to generate circuits.

When I am PhDone:

Inductive aexp : nat → Type :=

| AVar: $\forall n (i : \text{Var } E \ n), \text{aexp } n$
| AConst: $\forall n, \text{Word.word } n \rightarrow \text{aexp } n$
| APlus: $\forall n, \text{aexp } n \rightarrow \text{aexp } n \rightarrow \text{aexp } n$
| ALO: $\forall n \ m, \text{aexp } (n + m) \rightarrow \text{aexp } n$
| AHi: $\forall n \ m, \text{aexp } (n + m) \rightarrow \text{aexp } m$
| ACat: $\forall n \ m, \text{aexp } n \rightarrow \text{aexp } m \rightarrow \text{aexp } (n + m)$.

Inductive bexp : Type :=

| BTrue: bexp
| BFalse: bexp
| BEq: $\forall n, \text{aexp } n \rightarrow \text{aexp } n \rightarrow \text{bexp}$
| BLt: $\forall n, \text{aexp } n \rightarrow \text{aexp } n \rightarrow \text{bexp}$
| BNot: bexp → bexp
| BAnd: bexp → bexp → bexp.

Inductive com (E: list nat) : Type :=


| CSkip: com E
| CAss: $\forall n (v : \text{Var } E \ n), \text{aexp } E \ n \rightarrow \text{com } E$
| CSeq: com E → com E → com E
| CIIf: bexp E → com E → com E → com E
| CWhile: bexp E → com E → com E
| CNew: $\forall n, \text{aexp } E \ n \rightarrow \text{com } (\text{snoc } E \ n) \rightarrow \text{com } E$

One more word on Plugs

- Thanks to the use of tags, plugs can be defined by proof search.
- ... but, for each plug, we have to exhibit the function it implements (up to isos).
- A better solution for simple plugs is to use the following definition.

Inductive monoid : Type :=
 | Var : Type → monoid
 | • : monoid → monoid → monoid.

Inductive ⊢ : monoid → monoid → Set :=
 | M : ∀ A B C, A ⊢ C → B ⊢ C → (A • B) ⊢ C
 | L : ∀ A B C, A ⊢ B → A ⊢ (B • C)
 | R : ∀ A B C, A ⊢ B → A ⊢ (C • B)
 | I : ∀ A, A ⊢ A.

 

$\mathbb{C}(n \oplus m \oplus p)(p \oplus (n \oplus n))$

$$M \frac{R \frac{I}{p \vdash (n \bullet m) \bullet p} \quad L \frac{L \frac{M \frac{I \quad I}{n \bullet n \vdash n}}{n \bullet n \vdash n \bullet m}}{n \bullet n \vdash (n \bullet m) \bullet p}}{p \bullet (n \bullet n) \vdash (n \bullet m) \bullet p}$$


- Evaluated to $(p \oplus (n \oplus n)) \rightarrow (n \oplus m \oplus p)$ (the plug)
- Evaluated to $(\bar{n} \otimes \bar{m} \otimes \bar{p}) \rightarrow (\bar{p} \otimes (\bar{n} \otimes \bar{n}))$ (the action of the plug on values)

One more word on Plugs

- Thanks to the use of tags, plugs can be defined by proof search.
- ... but, for each plug, we have to exhibit the function it implements (up to isos).
- A better solution for simple plugs is to use the following definition.

Inductive monoid : Type :=
 | Var : Type → monoid
 | • : monoid → monoid → monoid.

Inductive ⊢ : monoid → monoid → Set :=
 | M : ∀ A B C, A ⊢ C → B ⊢ C → (A • B) ⊢ C
 | L : ∀ A B C, A ⊢ B → A ⊢ (B • C)
 | R : ∀ A B C, A ⊢ B → A ⊢ (C • B)
 | I : ∀ A, A ⊢ A.

 

$\mathbb{C}(n \oplus m \oplus p) (p \oplus (n \oplus n))$

$$M \frac{R \frac{I}{p \vdash (n \bullet m) \bullet p} \quad L \frac{L \frac{M \frac{I \quad I}{n \bullet n \vdash n}}{n \bullet n \vdash n \bullet m}}{n \bullet n \vdash (n \bullet m) \bullet p}}{p \bullet (n \bullet n) \vdash (n \bullet m) \bullet p}$$

- Evaluated to $(p \oplus (n \oplus n)) \rightarrow (n \oplus m \oplus p)$ (the plug)
- Evaluated to $(\bar{n} \otimes \bar{m} \otimes \bar{p}) \rightarrow (\bar{p} \otimes (\bar{n} \otimes \bar{n}))$ (the action of the plug on values)